

# CS507 : Verilog/VHDL

## Sequential Logic Assignment

Instructor: Dr. Sukarn Agarwal,  
Assistant Professor,  
School of Computing and Electrical Engineering,  
IIT Mandi

April 2, 2024

### Sequential Logic in Verilog

- Sequential Logic state transition is triggered by the “Clock” signal.
- Latches are sensitive to the level of signal.
- Flip Flop is sensitive to the transition of signal.

### New Verilog Construct for Sequential Logic

To model a sequential logic, two new programming constructs are required:

1. `always`
2. `posedge/negedge`

### The `always` block

The `always` block basic syntax are as follows:

```
always @ (sensivity list)
statement;
```

whenever the event in the `sensitivity list` occurs, the `statement` is executed.

### Sample Code Structure of D flip flop

```
module flop (input clk,
             input [3:0] d,
             output reg [3:0] q);
always @ (posedge clk)
q <= d;
endmodule
```

The detailed description of the above D flip flop module are as follows:

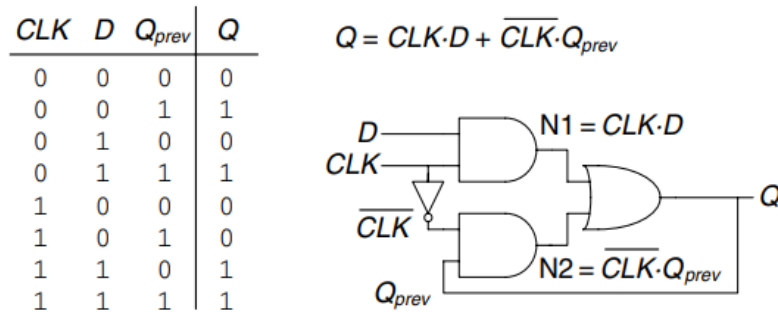


Figure 1: Improved Version of D Latch

- `posedge` defines a rising edge (transition from 0 to 1).
- Statement executed when the clock signal rises (i.e., on positive edge (`posedge`) of the clock (`clk`))
- Once the `clk` signal rises; the value of `d` is assigned to `q`.
- Note that `assign` statement is not used within an `always` block.
- Assigned variables need to be declared as `reg`.
- The name `reg` does not necessarily mean the value is a register.

With that sample coding D flip flop module in mind, implement the following Verilog programs using sequential logic construct.

### Problem Statements

#### Level-Easy

**Problem 1:** Implement a verilog module of an SR latch with asynchronous enable and reset.

**Problem 2:** Implement the Verilog module of an improved version of D latch as shown in figure 1. Specify delays of 1 ns to each gate. With your simulator, show that the latch operates correctly.

#### Level-Medium

**Problem 3:** Design a verilog module of counter that counts from 7 to 0 (e.g., 7, 6, 5, 4, 3, 2, 1, 0).

**Problem 4:** Implement a verilog module of UP/DOWN modulo 8 Gray Code Counter as shown in table 2, adding an Input UP. If UP = 1, the counter advances sequentially to the next number. Otherwise, UP = 0, the counter stays with the old value.

#### Level-Difficult

**Problem 5:** Implement a verilog module of N-bit bidirectional shift registers using D flip flop. (Hint: Use Parameterized Module to implement N).

Number	Gray code		
0	0	0	0
1	0	0	1
2	0	1	1
3	0	1	0
4	1	1	0
5	1	1	1
6	1	0	1
7	1	0	0

Figure 2: Gray Code Counter Table

**Problem 6:** Implement a single port memory of address space 128 and the addressability of 16-bit in Verilog. The memory has four inputs: clock, write enable, write address register, and read address register, and two outputs: read and write data register.

**Submission Format and Deadline:** Submit all your source code, test bench code, and output/waveform (if applicable) in a zipped format by the end of the day of 20 April 2024 (IST) at Moodle. Further, any copy case between the assignment(s) results in a zero mark. Note that TA may run the Plagiarism checker to check if the code is not copied from any other online source(s); if the tool finds more than a 30% match percentage, it results in a zero mark. In case of any doubt(s) regarding the assignment, you can contact me at [sukarn@iitmandi.ac.in](mailto:sukarn@iitmandi.ac.in).